

04 - Basic Arithmetic Blocks and Operations

- Adders
 - Half adder, Full adder, Word adder
 - Carry, ripple carry, look-ahead carry
- Subtraction
 - Using adders; carry logic
- Multiply
 - Parallel and serial multiply
- Division
 - Concept; implementation
- ALU
 - Accumulator, status flags

VHDL code for an 8x8 combinational multiplier

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;


entity mul_8x8 is
    port ( A: in  unsigned ( 7 downto 0 );
           B: in  unsigned ( 7 downto 0 );
           P: out unsigned (15 downto 0));
end mul8x8;

architecture arch of mul8x8 is
begin
    P <= A * B;
end arch;
```

Xilinx FPGAs Architecture

- All Xilinx FPGAs contain the same **basic resources**
 - **Logic Resources**
 - Slices (grouped into CLBs)
 - Contain combinatorial logic and register resources
 - Memory
 - **Multipliers**
 - **Interconnect Resources**
 - Programmable interconnect
 - IOBs
 - Interface between the FPGA and the outside world
 - **Other resources**
 - Global clock buffers
 - Boundary scan logic


Virtex-II Architecture

 

Virtex™-II architecture's core voltage operates at 1.5V


Carry Chains

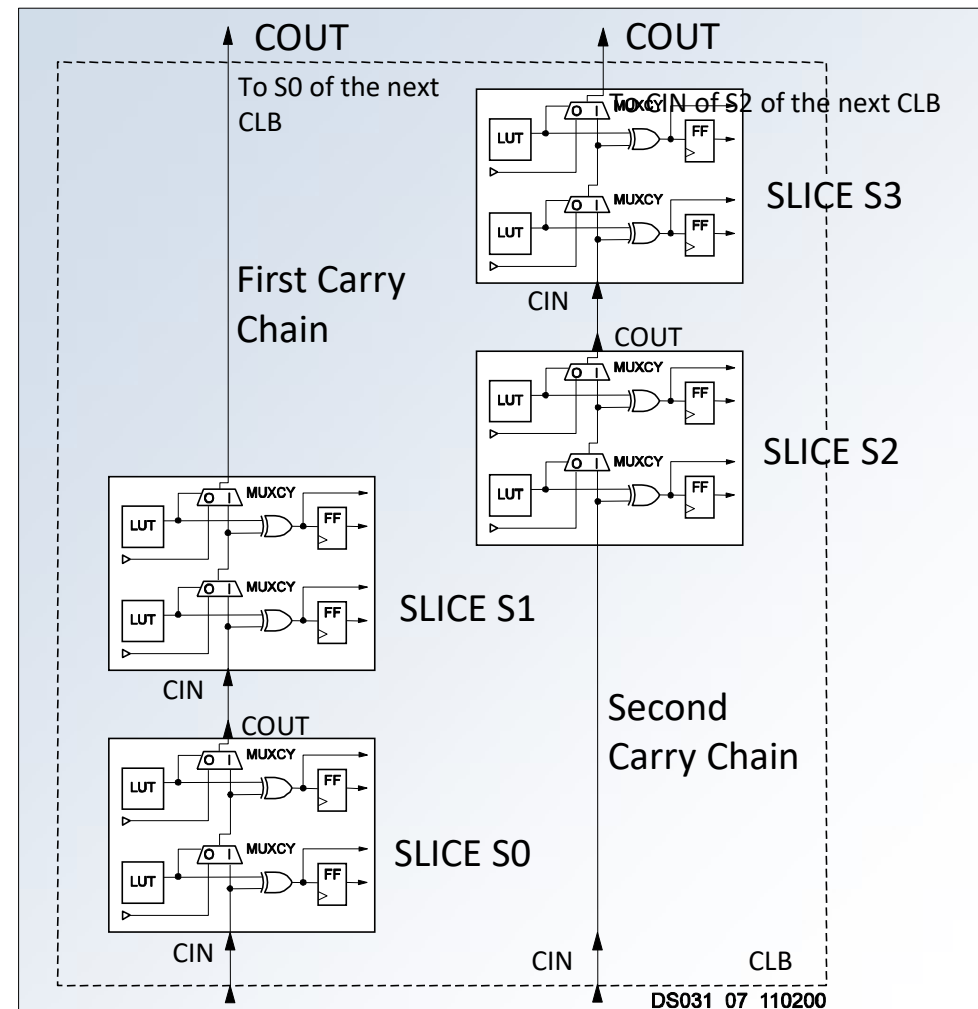- Simple, fast, and complete arithmetic Logic
 - Dedicated XOR gate for single-level sum completion
 - Uses dedicated routing resources
 - All synthesis tools can infer carry logic




Multiplier AND Gate

 - Highly efficient multiply and add implementation
 - Earlier FPGA architectures require two LUTs per bit to perform the multiplication and addition
 - The MULT_AND gate enables an area reduction by performing the *multiply* and the *add* in one LUT per bit



Embedded Multiplier Blocks

 - 18-bit two's complement signed operation
- Optimized to implement Multiply and Accumulate functions
- Multipliers are physically located next to block SelectRAM™ memory




The Spartan-3 Family


Built for high volume, low-cost applications



 **18x18 bit Embedded
Pipelined Multipliers for
efficient DSP**



 
**Up to eight on-chip Digital
Clock Managers to support
multiple system clocks**



Spartan-3



 
**Configurable 18K Block RAMs +
Distributed RAM**




**4 I/O Banks,
Support for
all I/O Standards
including
PCI, DDR333,
RSDS, mini-LVDS**

Xilinx Spartan 6 FPGA Architecture

Spartan-6 FPGA


 


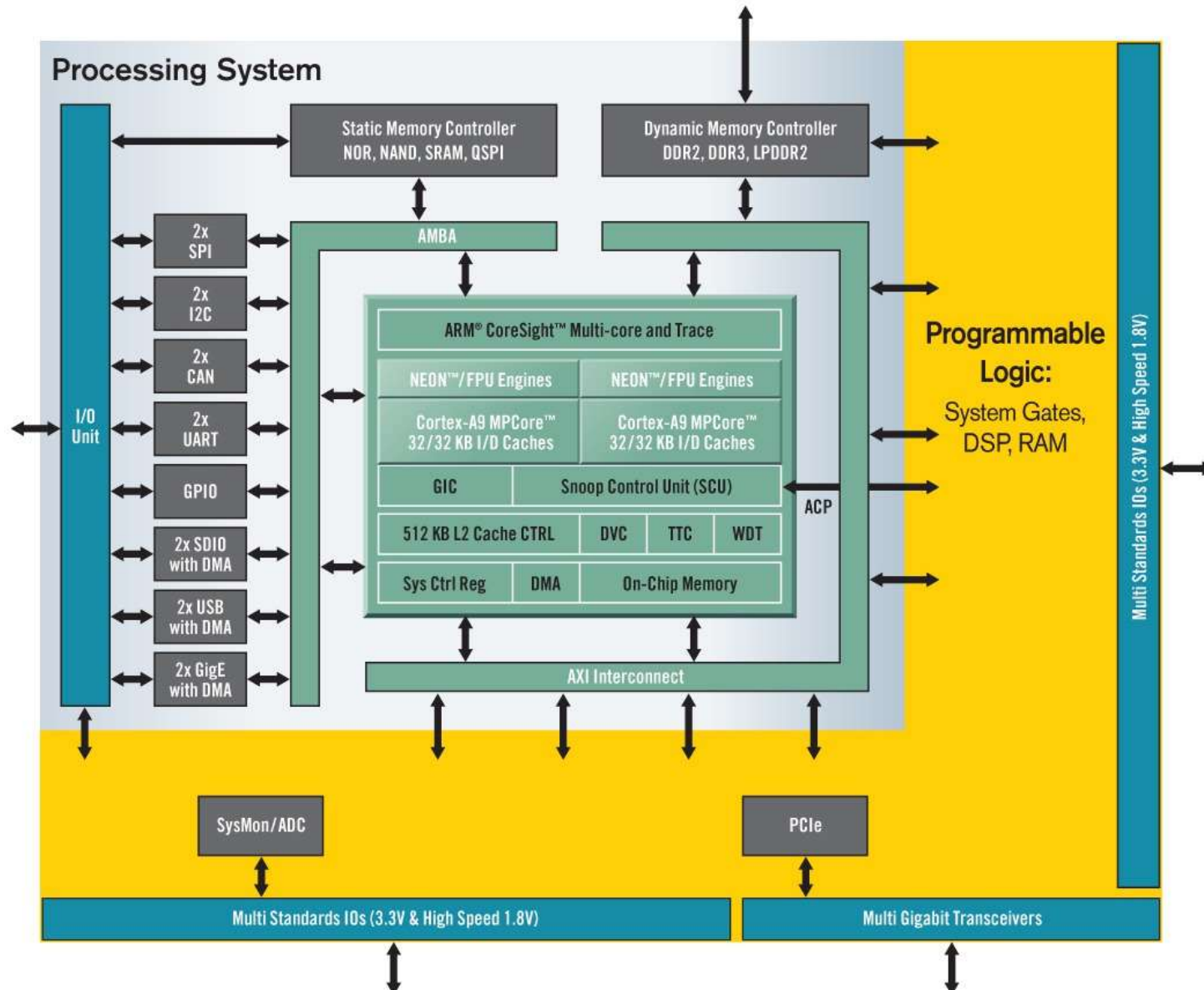Zynq All Programmable SoC System Architecture



PYNQ: PYTHON PRODUCTIVITY

- <http://www.pynq.io/board.html>

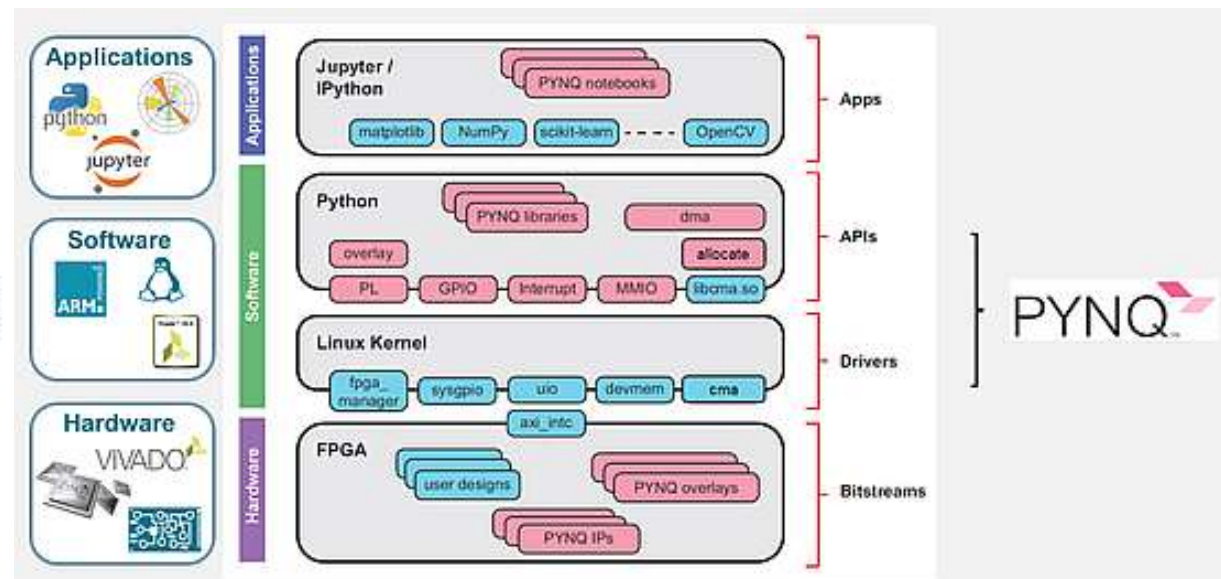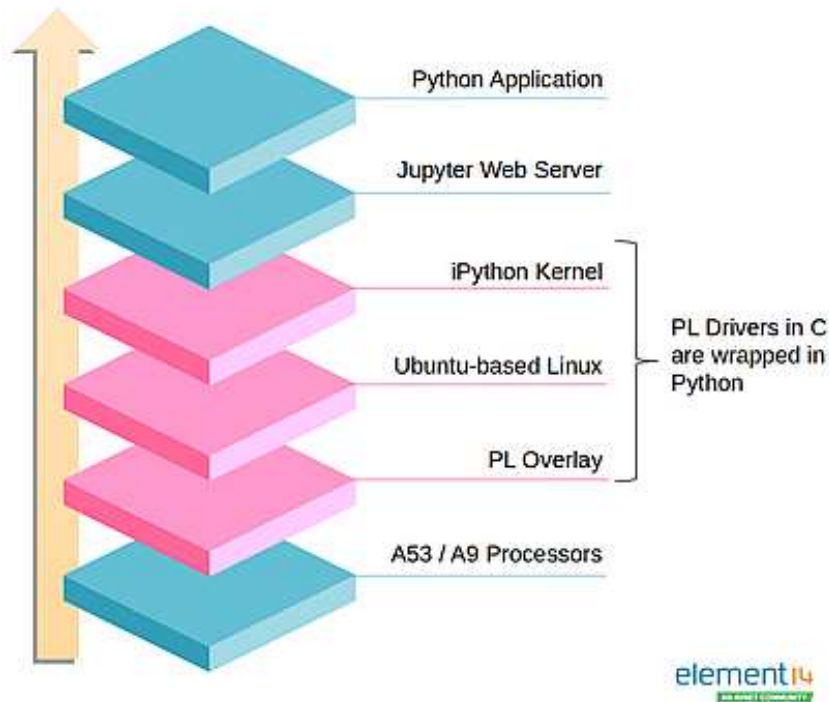

ALU

Arithmetic Logic Unit - ALU

- Mathematician John von Neumann proposed the ALU concept in 1945.
- an ALU is a digital circuit that performs:
 - arithmetic operations and
 - logical operations


Legend

A, B – Operands (Registers, Data)



R – Result

F – Instruction code

D – Output status (Flags)

 

Simple ALU – Block Diagram

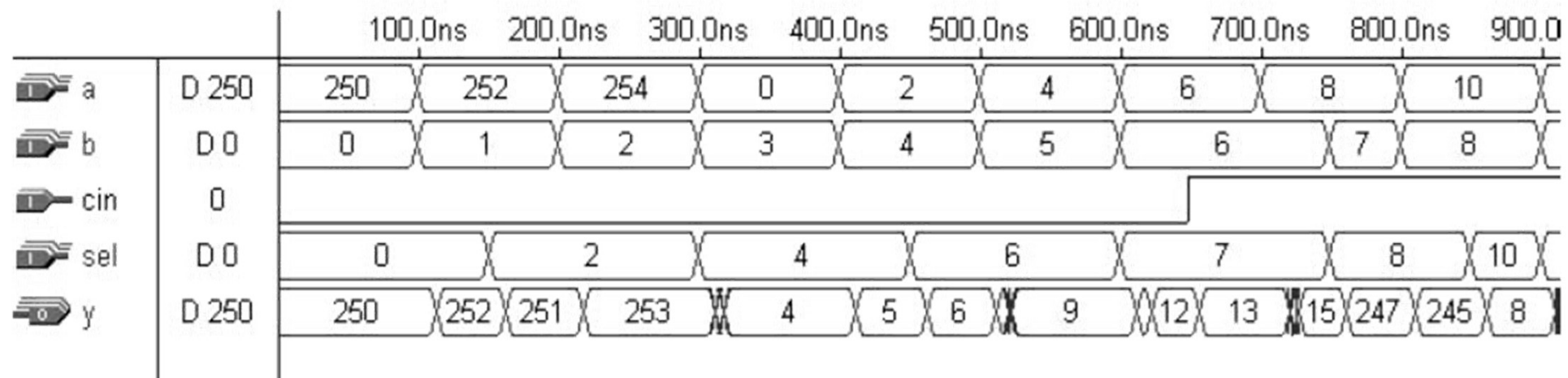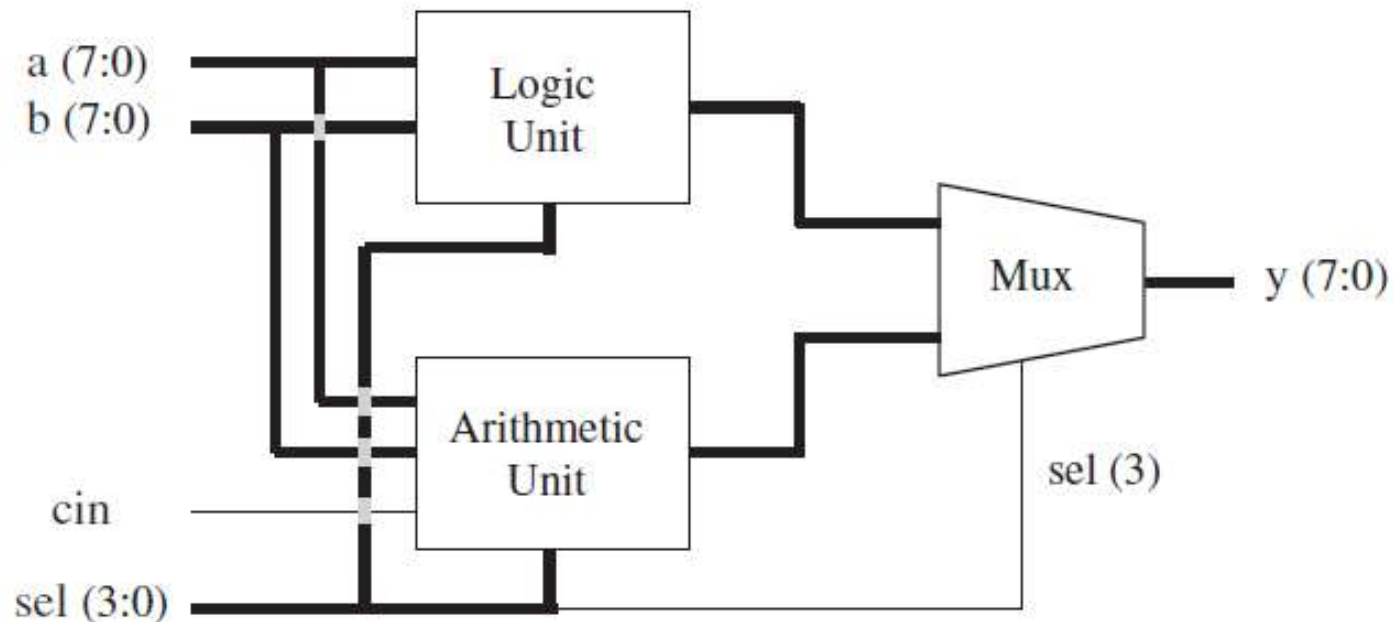

ALU

sel	Operation	Function	Unit
0000	$y \leq a$	Transfer a	Arithmetic
0001	$y \leq a + 1$	Increment a	
0010	$y \leq a - 1$	Decrement a	
0011	$y \leq b$	Transfer b	
0100	$y \leq b + 1$	Increment b	
0101	$y \leq b - 1$	Decrement b	
0110	$y \leq a + b$	Add a and b	
0111	$y \leq a + b + C_{in}$	Add a and b with carry	
1000	$y \leq \text{not } a$	Complement a	Logic
1001	$y \leq \text{not } b$	Complement b	
1010	$y \leq a \text{ and } b$	AND	
1011	$y \leq a \text{ or } b$	OR	
1100	$y \leq a \text{ nand } b$	NAND	
1101	$y \leq a \text{ nor } b$	NOR	
1110	$y \leq a \text{ xor } b$	XOR	
1111	$y \leq a \text{ xnor } b$	XNOR	

ALU – VHDL Code (Entity)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity ALU is
port (a, b: in  std_logic_vector (7 downto 0);
      sel: in  std_logic_vector (3 downto 0);
      cin: in  std_logic;
      y: out std_logic_vector (7 downto 0));
end ALU;

architecture dataflow of ALU is
    signal arith, logic: std_logic_vector (7 downto 0);
begin
```


ALU – VHDL Code (Architecture)

----- Arithmetic unit: -----

```
with sel(2 downto 0) select
    arith <= a when "000",
             a+1 when "001",
             a-1 when "010",
             b  when "011",
             b+1 when "100",
             b-1 when "101",
             a+b when "110",
             a+b+cin when others;
```

----- Logic unit: -----


```
with sel(2 downto 0) select
    logic <= not a when "000",
             not b when "001",
             a and b when "010",
             a or b when "011",
             a nand b when "100",
             a nor b when "101",
             a xor b when "110",
             not (a xor b) when others;
```

----- Mux: -----


```
with sel(3) select
    y <= arith when '0',
         logic when others;

end dataflow;
```

Mid-Range PIC Block Diagram

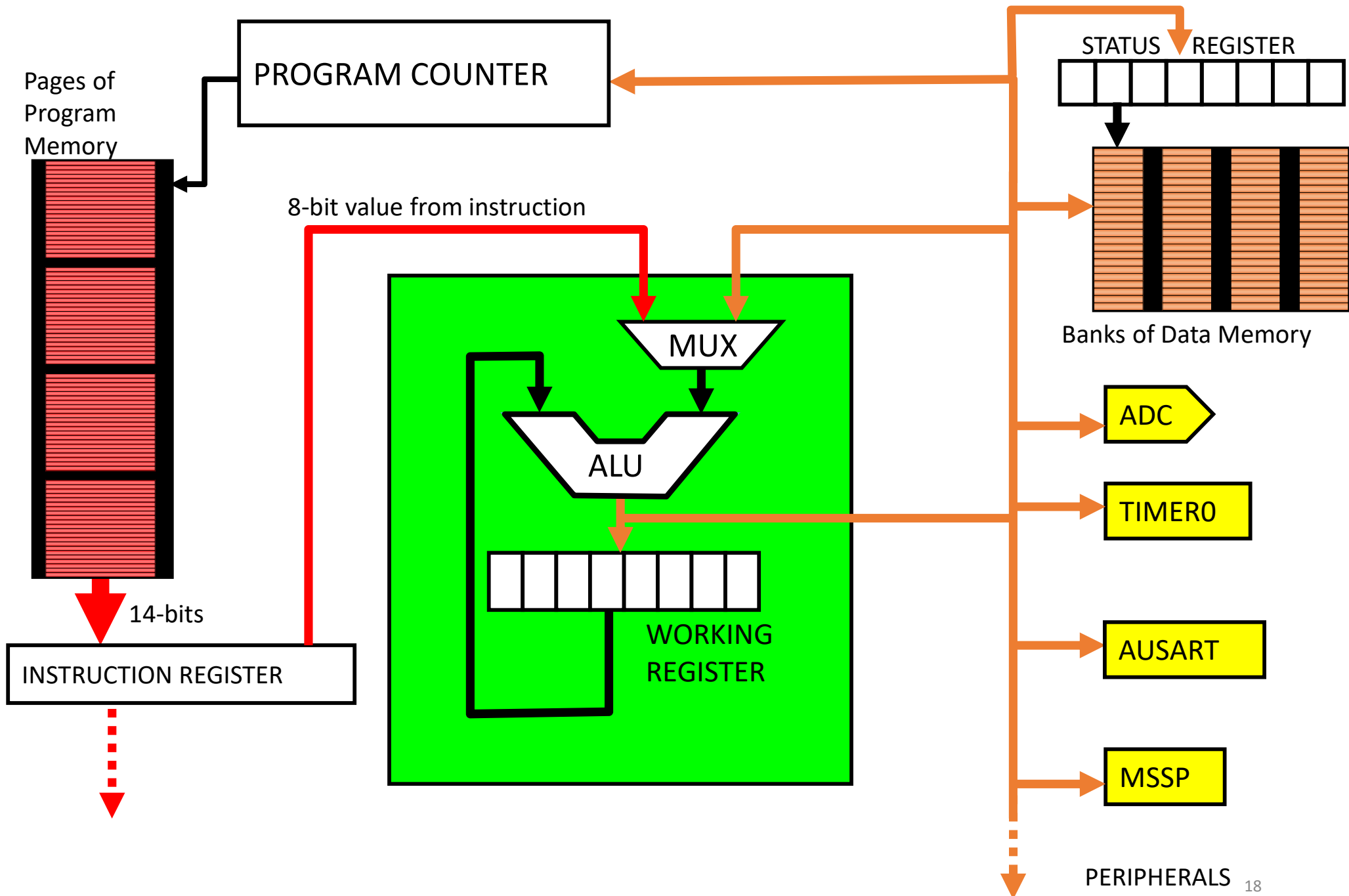

STATUS Register

 

IRP: Register Bank Select (used for Indirect addressing)

0 = Bank 0, 1 1 = Bank 2, 3

RP1:RP0: Register Bank Select Bits (used for direct addressing)

00 = Bank 0, 01 = Bank 1, 10 = Bank 2, 11 = Bank 3

$\overline{\text{TO}}$: Time-out bit

0 = A WDT time-out occurred

$\overline{\text{PD}}$: Power-down bit

0 = SLEEP instruction executed

Z: Zero bit

1 = Result of arithmetic operation is zero


DC: Digit carry / borrow bit

1 = Carry out of 4th low order bit occurred / No borrow occurred

C: Carry / borrow bit

1 = Carry out of MSb occurred / No borrow occurred

Status Register

 

RP1	RP0	
0	0	BANK0
0	1	BANK1
1	0	BANK2
1	1	BANK3

CCR = Condition Code Register

- Contains:
 - Arithmetic status of the ALU
 - The RESET status
 - Bank select bits for data memory

Indirect Register Bank Select bit:
(used for indirect addressing)

1 = Bank 2,3

0 = Bank 0,1